

BASIC

ELECTRONICS

{22225}


# Seven-Segment display

A seven-segment display (SSD), or seven-segment indicator, is a form of electronic display device for displaying decimal numerals that is an alternative to the more complex dot matrix displays.

Seven-segment displays are widely used in digital clocks, electronic meters, basic calculators, and other electronic devices that display numerical information.

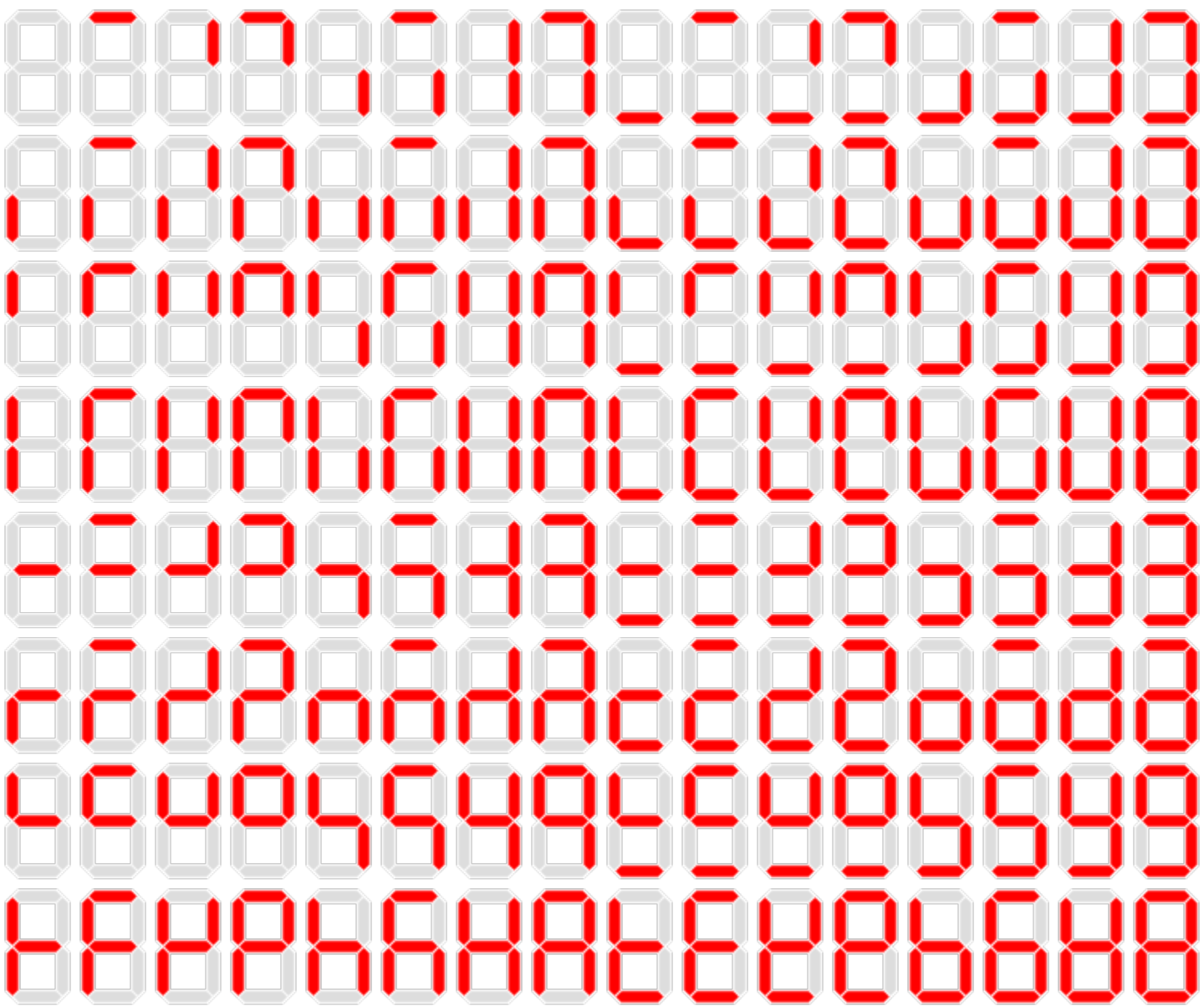An LED or Light Emitting Diode, is a solid state optical pn-junction diode which emits light energy in the form of photons.





**16x8 grid showing the  
all 128 states of a  
seven-segment display**

The emission of these photons occurs when the diode junction is forward biased by an external voltage allowing current to flow across its junction, and in Electronics we call this process electroluminescence. The actual colour of the visible light emitted by an LED, ranging from blue to red to orange, is decided by the spectral wavelength of the emitted light which itself is dependent upon the mixture of the various impurities added to the semiconductor materials used to produce it.

## 7-segment Display

Light emitting diodes have many advantages over traditional bulbs and lamps, with the main ones being their small size, long life, various colours, cheapness and are readily available, as well as being easy to interface with various other electronic components and digital circuits.

But the main advantage of light emitting diodes is that because of their small die size, several of them can be connected together within one small and compact package producing what is generally called a **7-segment Display**.

The *7-segment display*, also written as “seven segment display”, consists of seven LEDs (hence its name) arranged in a rectangular fashion as shown. Each of the seven LEDs is called a segment because when illuminated the segment forms part of a numerical digit (both Decimal and Hex) to be displayed. An additional 8th LED is sometimes used within the same package thus allowing the indication of a decimal point, (DP) when two or more 7-segment displays are connected together to display numbers greater than ten.


Each one of the seven LEDs in the display is given a positional segment with one of its connection pins being brought straight out of the rectangular plastic package. These individually LED pins are labelled from a through to g representing each individual LED. The other LED pins are connected together and wired to form a common pin.

So by forward biasing the appropriate pins of the LED segments in a particular order, some segments will be light and others will be dark allowing the desired character pattern of the number to be generated on the display. This then allows us to display each of the ten decimal digits 0 through to 9 on the same 7-segment display.

The displays common pin is generally used to identify which type of 7-segment display it is. As each LED has two connecting pins, one called the “Anode” and the other called the “Cathode”, there are therefore two types of LED 7-segment display called: **Common Cathode (CC)** and **Common Anode (CA)**.


The difference between the two displays, as their name suggests, is that the common cathode has all the cathodes of the 7-segments connected directly together and the common anode has all the anodes of the 7-segments connected together and is illuminated as follows.

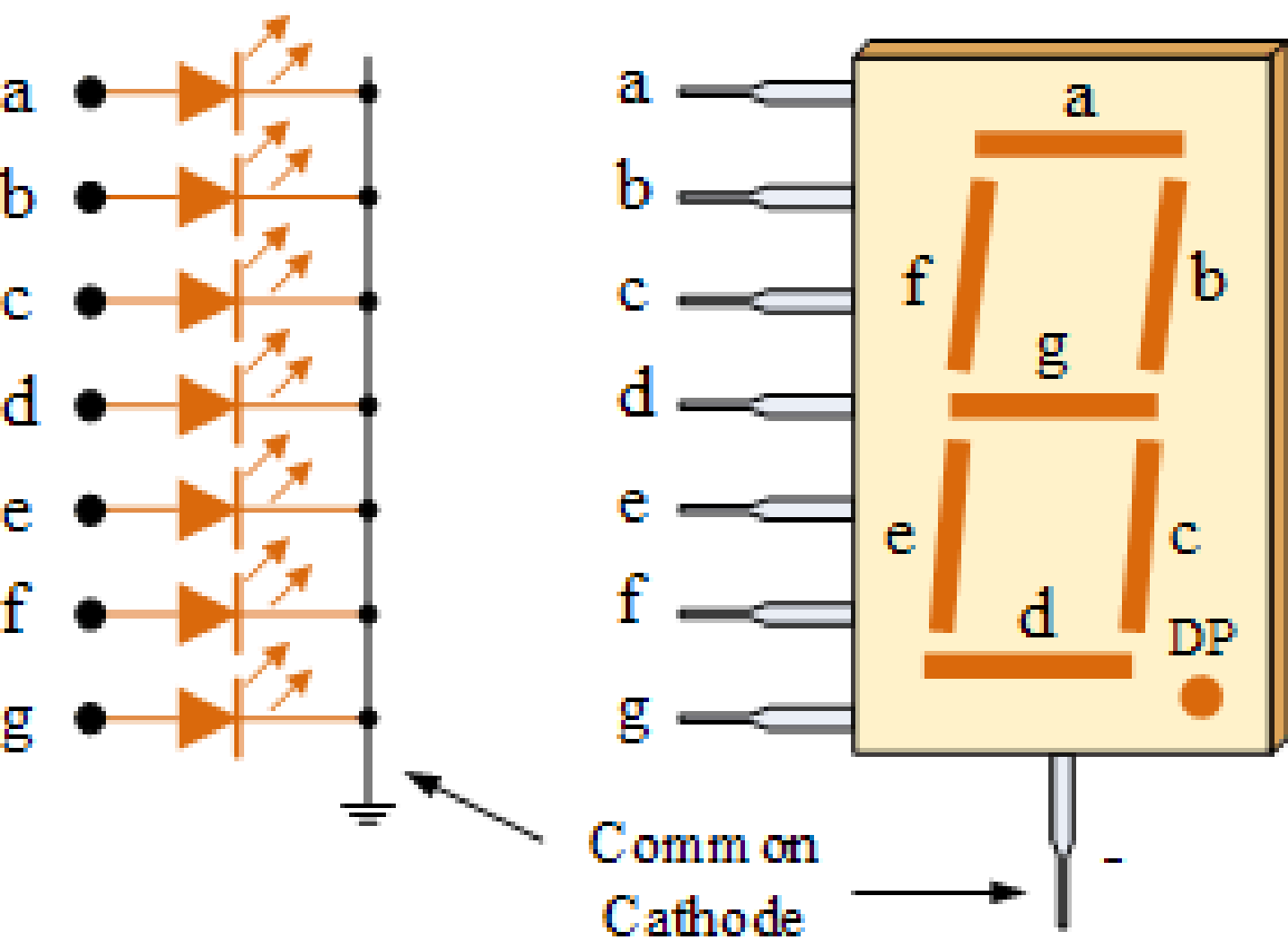1. The Common Cathode (CC) - In the common cathode display, all the cathode connections of the LED segments are joined together to logic "0" or ground. The individual segments are illuminated by application of a "HIGH", or logic "1" signal via a current limiting resistor to forward bias the individual Anode terminals (a-g).



Common Cathode 7-segment Display

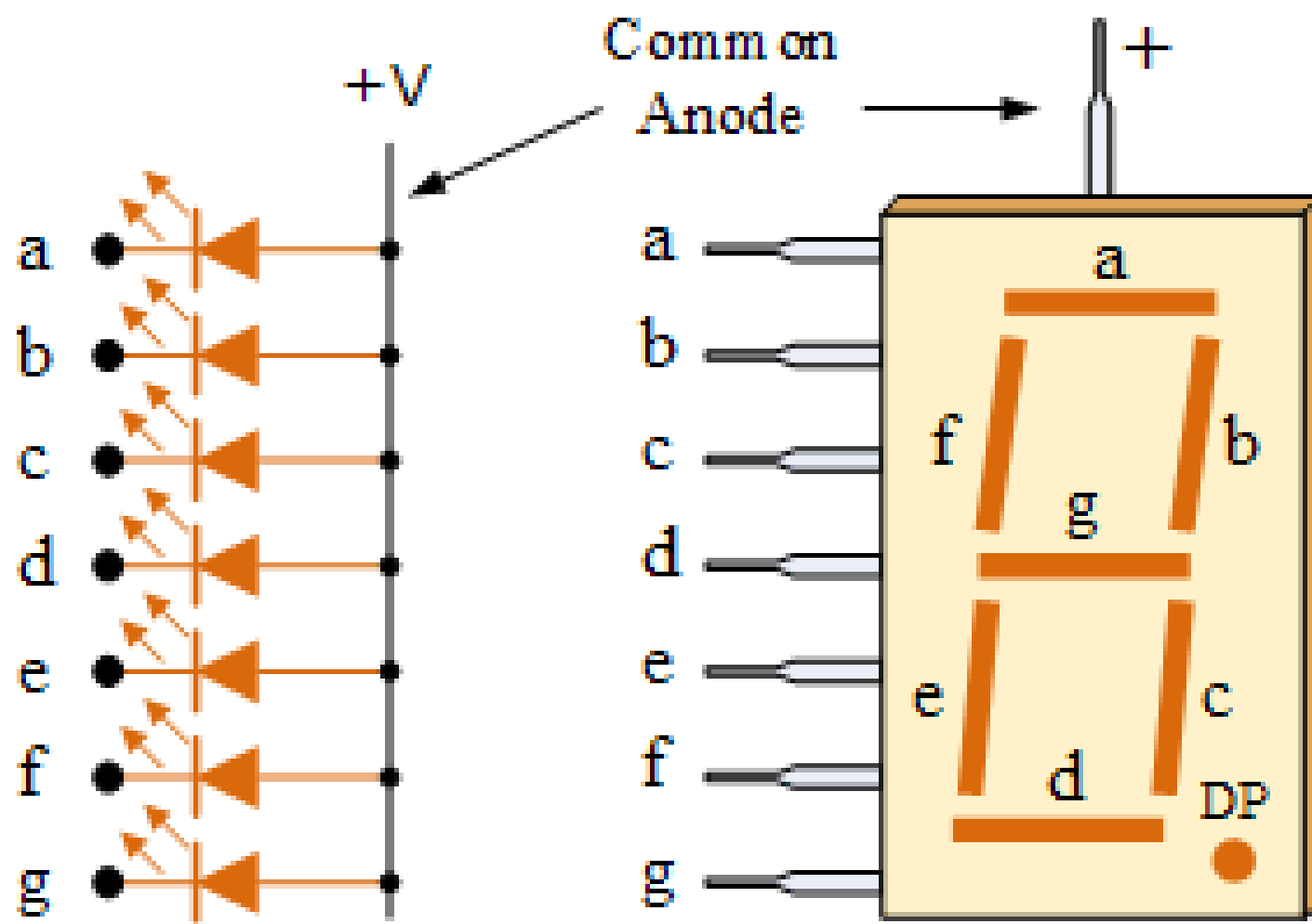
2. The Common Anode (CA) - In the common anode display, all the anode connections of the LED segments are joined together to logic “1”. The individual segments are illuminated by applying a ground, logic “0” or “LOW” signal via a suitable current limiting resistor to the Cathode of the particular segment (a-g).



Common Anode 7-segment Display

In general, common anode displays are more popular as many logic circuits can sink more current than they can source. Also note that a common cathode display is not a direct replacement in a circuit for a common anode display and vice versa, as it is the same as connecting the LEDs in reverse, and hence light emission will not take place.

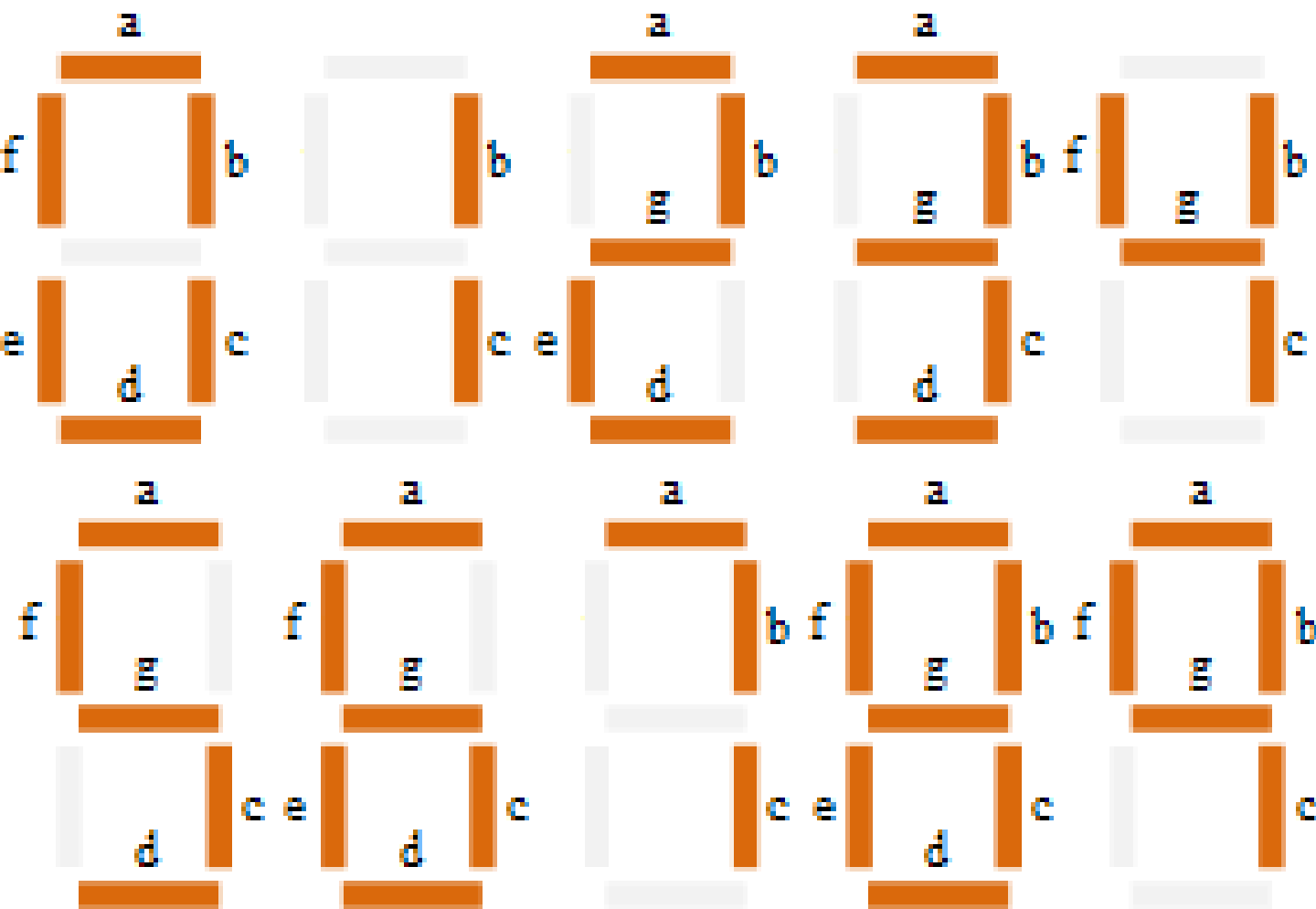Depending upon the decimal digit to be displayed, the particular set of LEDs is forward biased. For instance, to display the numerical digit 0, we will need to light up six of the LED segments corresponding to a, b, c, d, e and f. Thus the various digits from 0 through 9 can be displayed using a 7-segment display as shown.



7-Segment Display Segments for all Numbers





Then for a 7-segment display, we can produce a truth table giving the individual segments that need to be illuminated in order to produce the required decimal digit from 0 through 9 as shown below.

Decimal Digit	Individual Segments Illuminated						
	a	b	c	d	e	f	g
0	x	x	x	x	x	x	
1		x	x				
2	x	x		x	x		x
3	x	x	x	x			x
4		x	x			x	x
5	x		x	x		x	x
6	x		x	x	x	x	x
7	x	x	x				
8	x	x	x	x	x	x	x
9	x	x	x			x	x

## Driving a 7-segment Display


Although a 7-segment display can be thought of as a single display, it is still seven individual LEDs within a single package and as such these LEDs need protection from over current. LEDs produce light only when it is forward biased with the amount of light emitted being proportional to the forward current. This means then that an LEDs light intensity increases in an approximately linear manner with an increasing current. So this forward current must be controlled and limited to a safe value by an external resistor to prevent damage to the LED segments.

The forward voltage drop across a red LED segment is very low at about 2-to-2.2 volts, (blue and white LEDs can be as high as 3.6 volts) so to illuminate correctly, the LED segments should be connected to a voltage source in excess of this forward voltage value with a series resistance used to limit the forward current to a desirable value.

Typically for a standard red coloured 7-segment display, each LED segment can draw about 15 mA to illuminated correctly, so on a 5 volt digital logic circuit, the value of the current limiting resistor would be about  $200\Omega$   $(5v - 2v)/15mA$ , or  $220\Omega$  to the nearest higher preferred value.

So to understand how the segments of the display are connected to a  $220\Omega$  current limiting resistor consider the circuit below.

## Driving a 7-segment Display

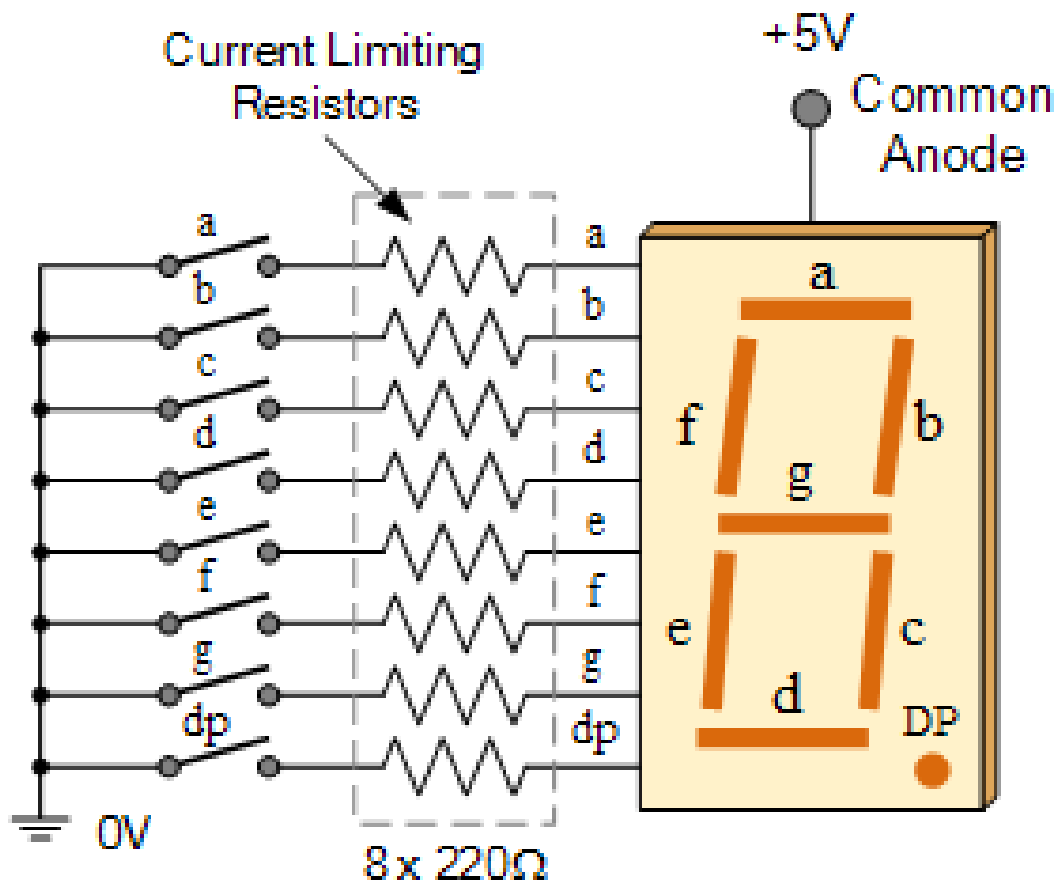

In this example, the segments of a common anode display are illuminated using the switches. If switch 'a' is closed, current will flow through the "a" segment of the LED to the current limiting resistor connected to pin 'a' and to 0 volts, making the circuit. Then only segment 'a' will be illuminated. So a LOW condition (switch to ground) is required to activate the LED segments on this common anode display.


But suppose we want the decimal number "4" to illuminate on the display. Then switches 'b', 'c', 'f' and 'g' would be closed to light the corresponding LED segments. Likewise for a decimal number "7", switches 'a', 'b', 'c' would be closed. But illuminating 7-segment displays using individual switches is not very practical.



7-segment Displays are usually driven by a special type of integrated circuit (IC) commonly known as a 7-segment decoder/driver, such as the CMOS 4511. This 7-segment display driver which is known as a Binary Coded Decimal or BCD to 7-segment display decoder and driver, is able to illuminate both common anode or common cathode displays. But there are many other single and dual display drivers available such as the very popular TTL 7447.

This BCD-to-7 segment decoder/driver takes a four-bit BCD input labelled A, B, C and D for the digits of the binary weighting of 1, 2, 4 and 8 respectively, has seven outputs that will pass current through the appropriate segments to display the decimal digit of the numeric LED display.


The digital outputs of the CD4511 are different from the usual CMOS outputs because they can provide up to 25mA of current each to drive the LED segments directly allowing different coloured LED displays to be used and driven.
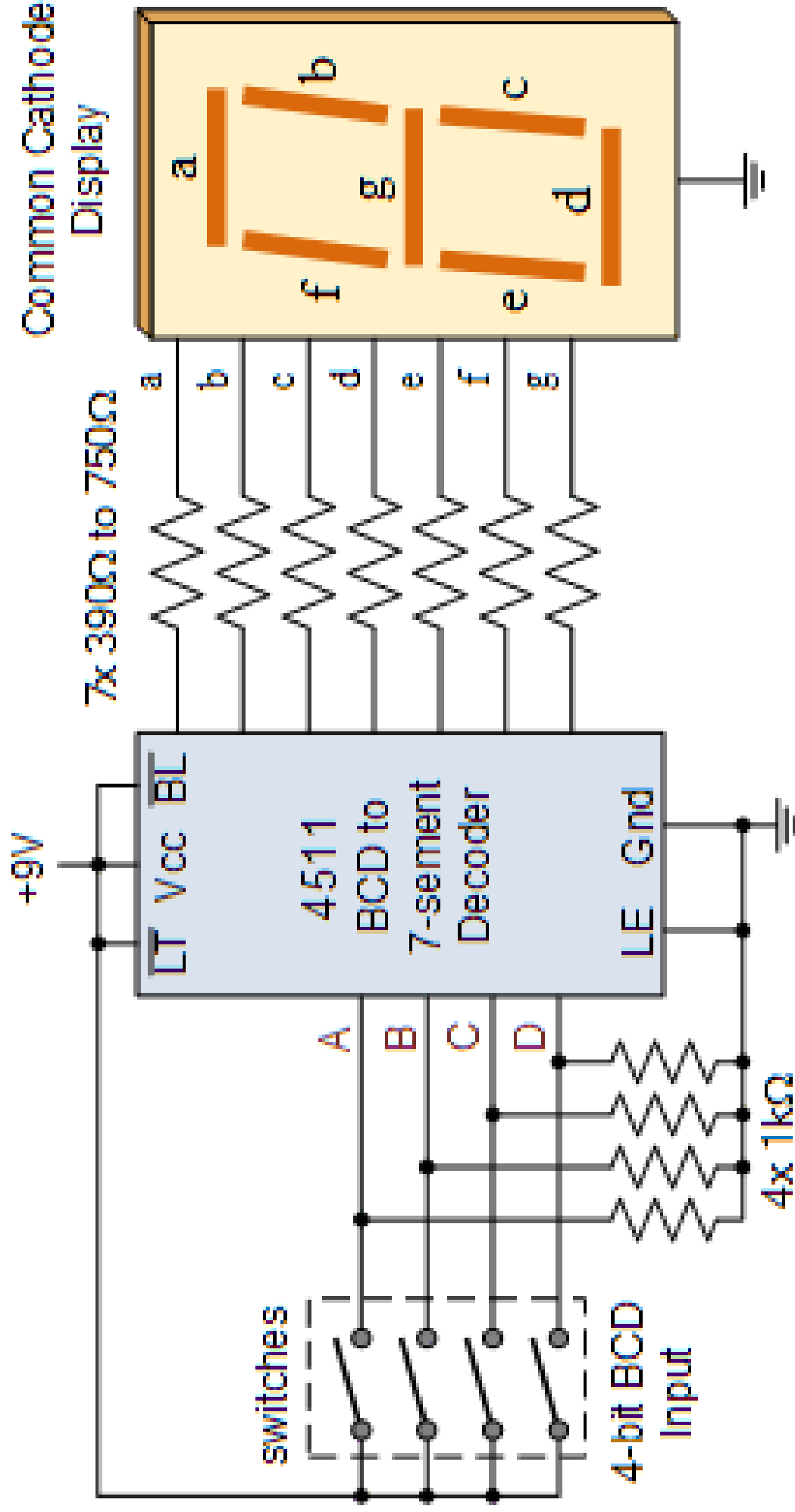
## Driving a 7-segment Display using a 4511



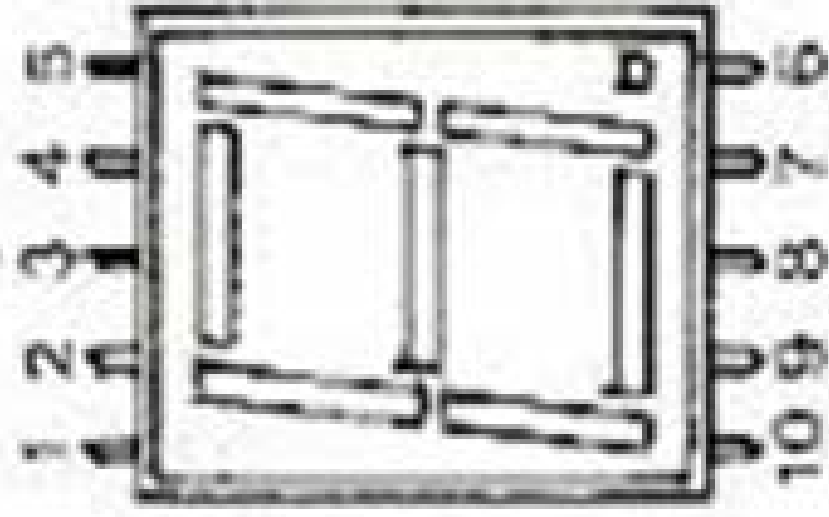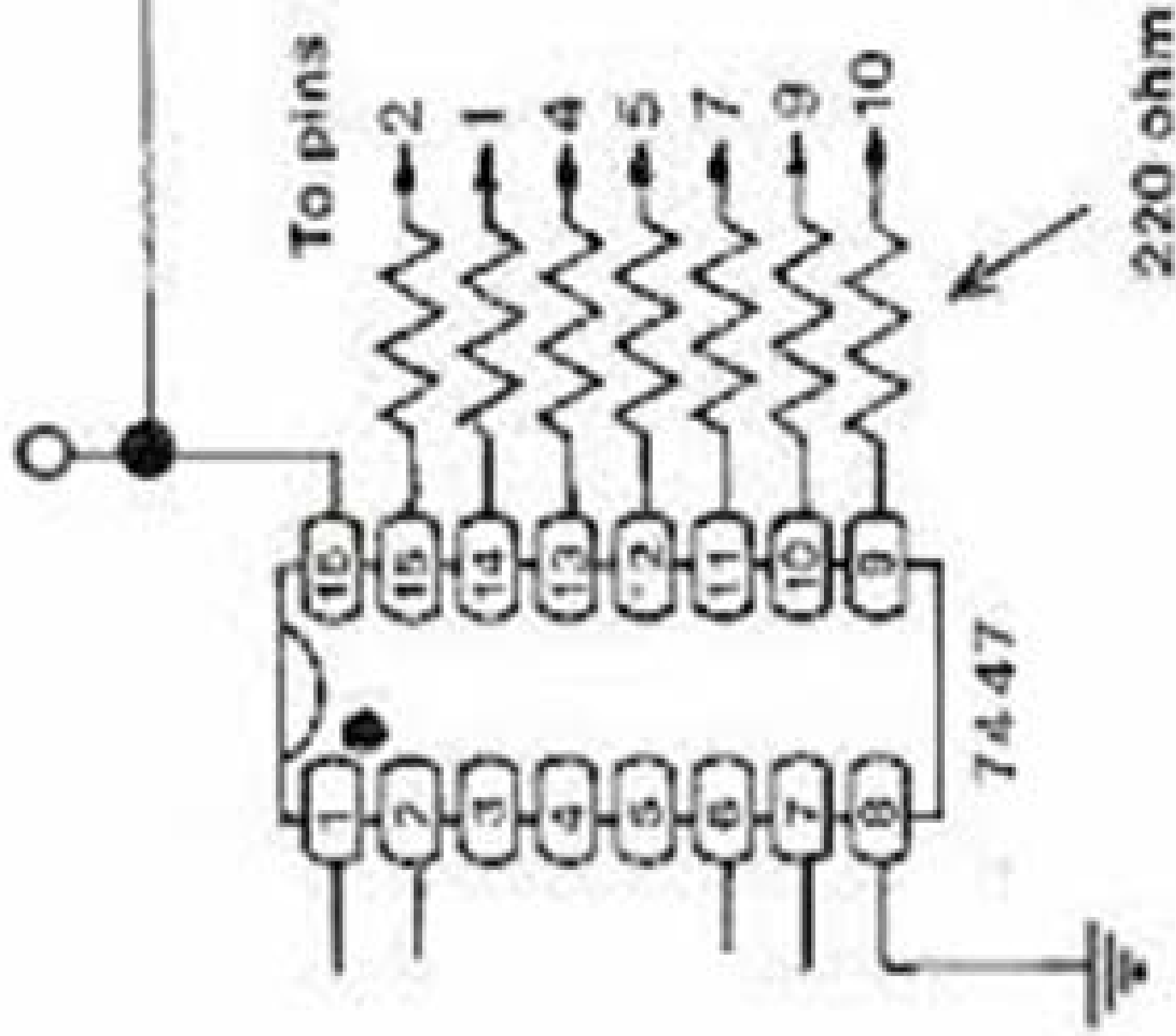



FND 510 Readout

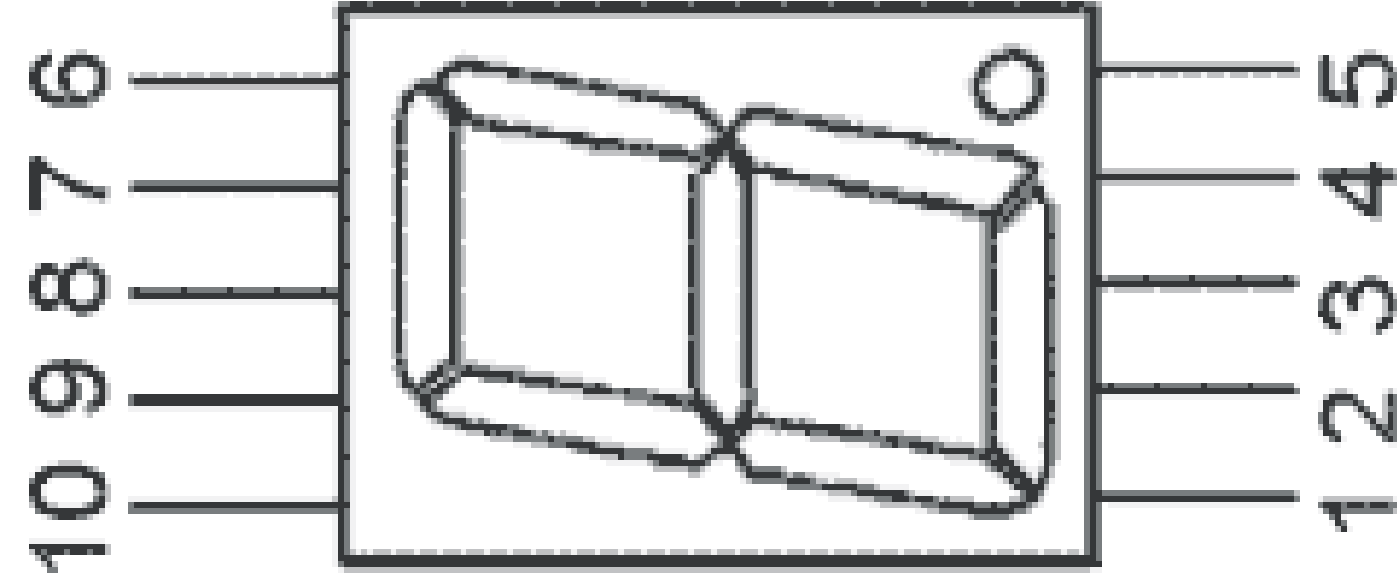


PIN NO.	MAN6960 E
1	Cathode E
2	Cathode D
3	Com. Anode
4	Cathode C
5	Cathode D.P.
6	Cathode B
7	Cathode A
8	Com. Anode
9	Cathode F
10	Cathode G



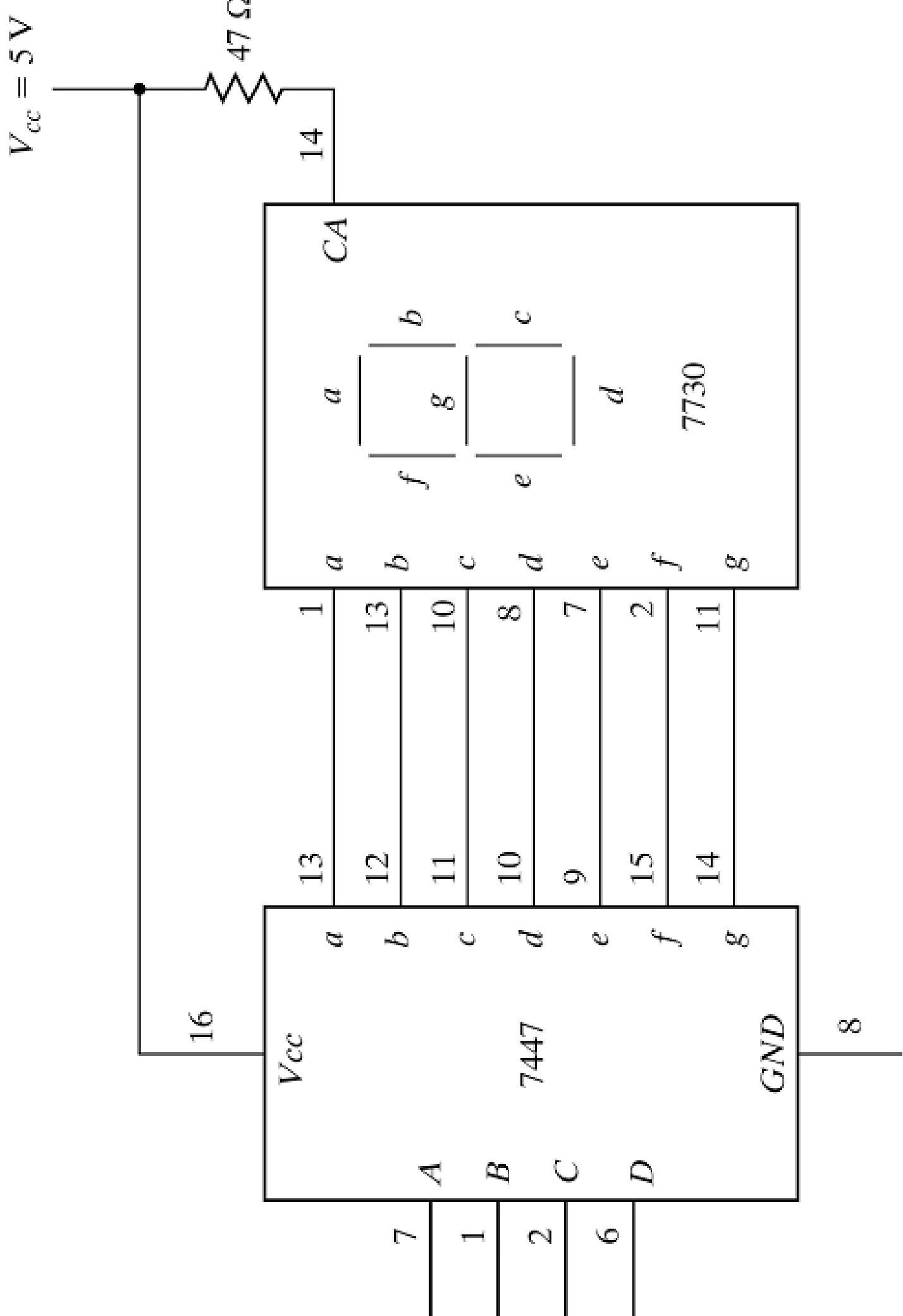

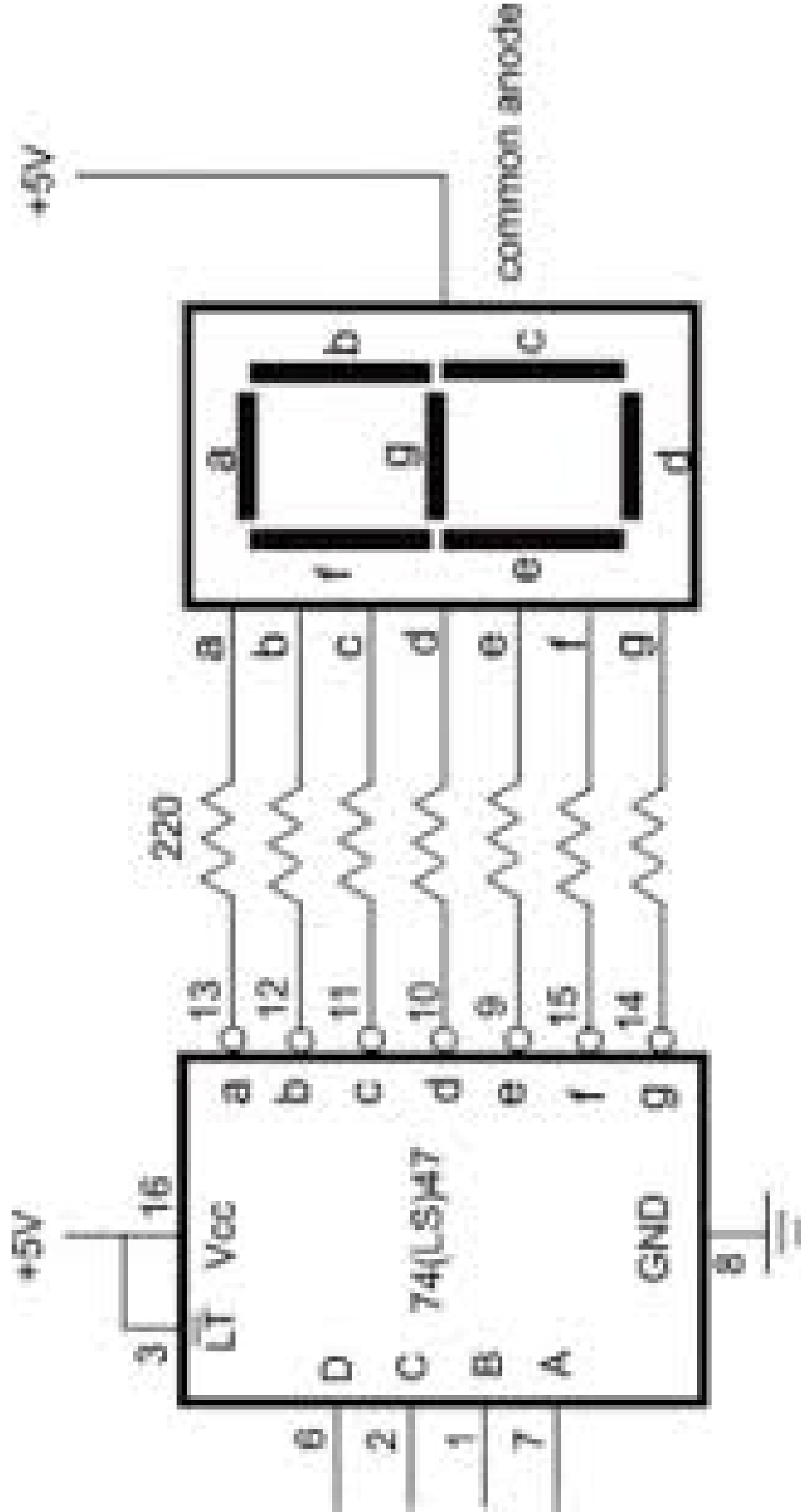

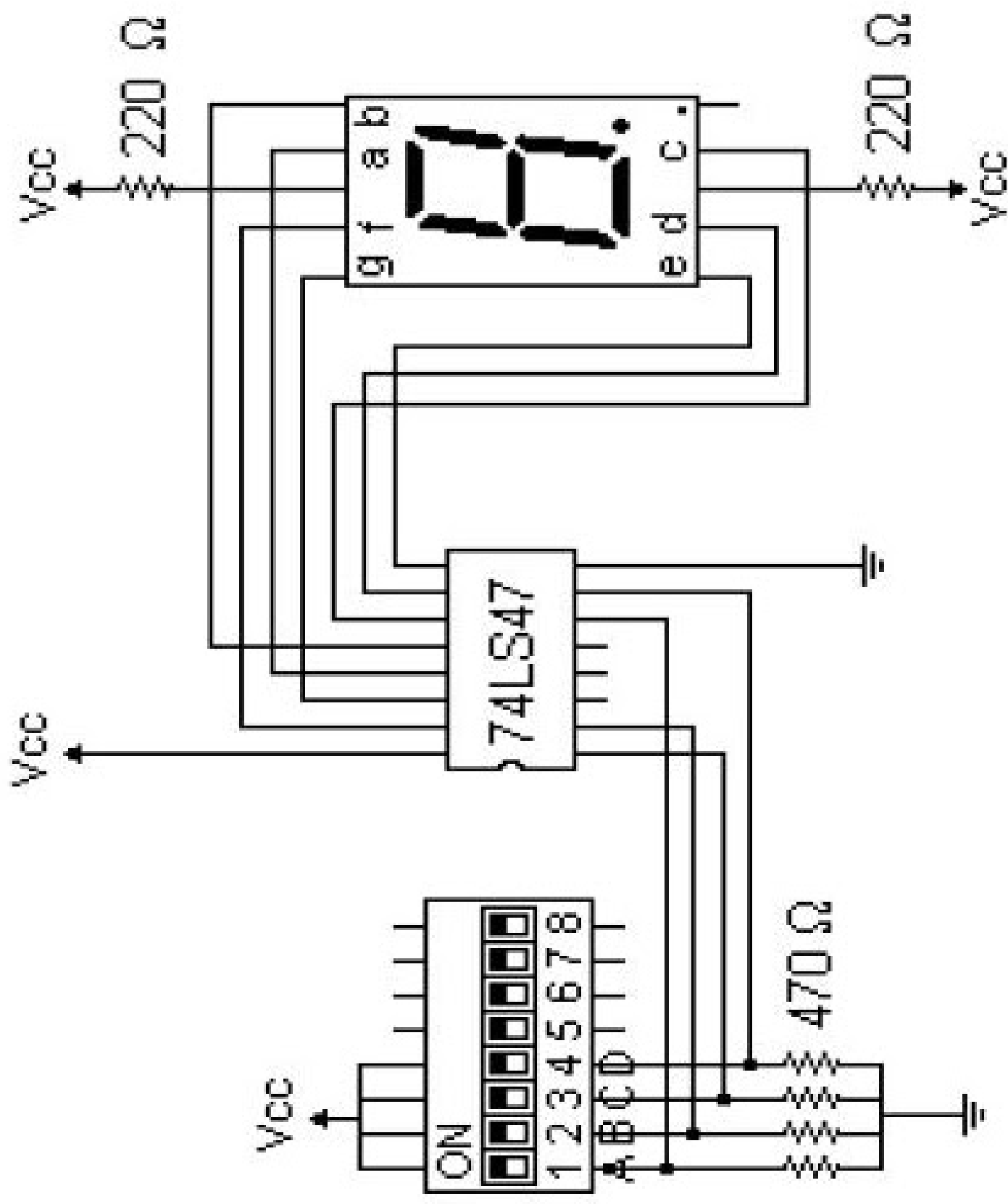

In this simple circuit, each LED segment of the common cathode display has its own anode terminal connected directly to the 4511 driver with its cathodes connected to ground. The current from each output passes through a  $1k\Omega$  resistor that limits it to a safe amount. The binary input to the 4511 is via the four switches. Then we can see that using a BCD to 7-segment display driver such as the CMOS 4511, we can control the LED display using just four switches (instead of the previous 8) or a 4-bit binary signal allowing up to 16 different combinations.

Most digital equipment use 7-segment Displays for converting digital signals into a form that can be displayed and understood by the user. This information is often numerical data in the form of numbers, characters and symbols. Common anode and common cathode seven-segment displays produce the required number by illuminating the individual segments in various combinations.

LED based 7-segment displays are very popular amongst Electronics hobbyists as they are easy to use and easy to understand. In most practical applications, 7-segment displays are driven by a suitable decoder/driver IC such as the CMOS 4511 or TTL 7447 from a 4-bit BCD input. Today, LED based 7-segment displays have been largely replaced by liquid crystal displays (LCDs) which consume less current.